

Universal Shift Register

Mohammed Latif Siddiq
Nadia Anjum

Bangladesh University of Engineering and Technology

July 15, 2018

Table of Contents

- 1 Introduction
- 2 Block Diagram
- 3 Components of Universal Shift Register
- 4 Circuit Diagram of Universal Shift Register
- 5 Uses of Universal Shift Register


Universal Shift Register is a register which can capable to transfer data in both the shift-right and shift-left, along with the necessary input and output terminals for parallel transfer.

Universal Shift Register has two functions -

- Bidirectional Shifting
- Parallel Loading

Block Diagram

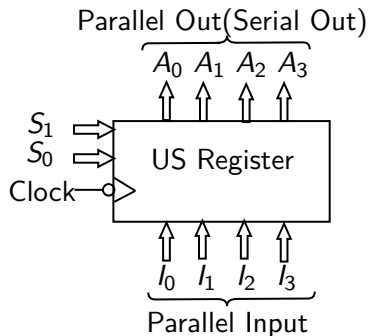
Block diagram and selection bits for 4 bit universal shift register :



S_1	S_0	Register Operation
0	0	No change
0	1	Shift Right
1	0	Shift Left
1	1	Parallel Load

Block Diagram

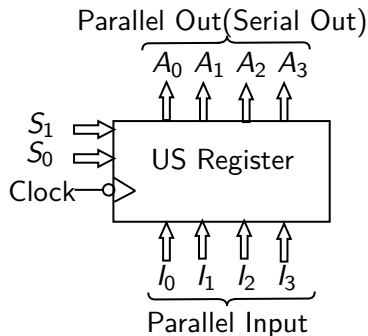
Block diagram and selection bits for 4 bit universal shift register :



S_1	S_0	Register Operation
0	0	No change
0	1	Shift Right
1	0	Shift Left
1	1	Parallel Load

Block Diagram

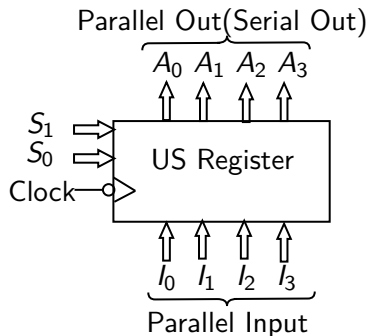
Block diagram and selection bits for 4 bit universal shift register :



S_1	S_0	Register Operation
0	0	No change
0	1	Shift Right
1	0	Shift Left
1	1	Parallel Load

Block Diagram

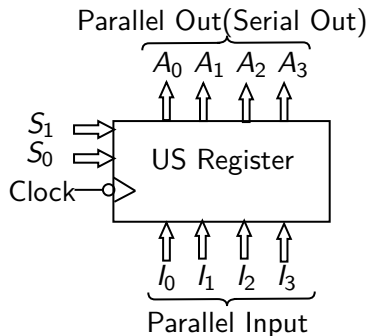
Block diagram and selection bits for 4 bit universal shift register :



S_1	S_0	Register Operation
0	0	No change
0	1	Shift Right
1	0	Shift Left
1	1	Parallel Load

Block Diagram

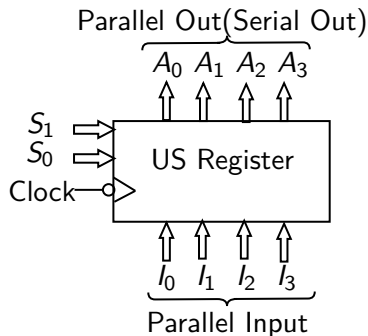Block diagram and selection bits for 4 bit universal shift register :



S_1	S_0	Register Operation
0	0	No change
0	1	Shift Right
1	0	Shift Left
1	1	Parallel Load

Components of Universal Shift Register


Universal Shift Register has two main components -

- 4 to 1 Multiplexer
- D Flip-Flop

Components of Universal Shift Register

- 4 to 1 Multiplexer

4-to-1 Multiplexer (MUX)

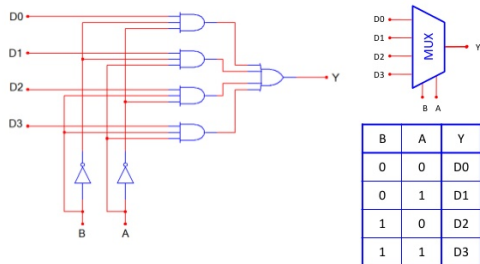

6

Components of Universal Shift Register

- D Flip-Flop

D Flip-flop


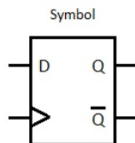


Table of truth:

clk	D	Q	\bar{Q}
0	0	Q	\bar{Q}
0	1	Q	\bar{Q}
1	0	0	1
1	1	1	0

Circuit Diagram

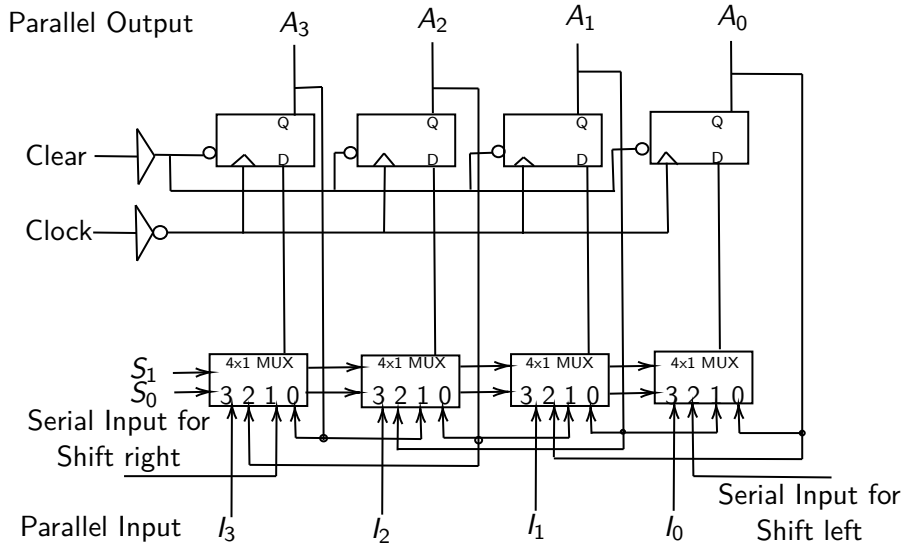
Circuit diagram for 4 bit universal shift register



Unchanged of Output in Universal Shift Register


When $S_0 = 0$ and $S_1 = 0$, output will changed.

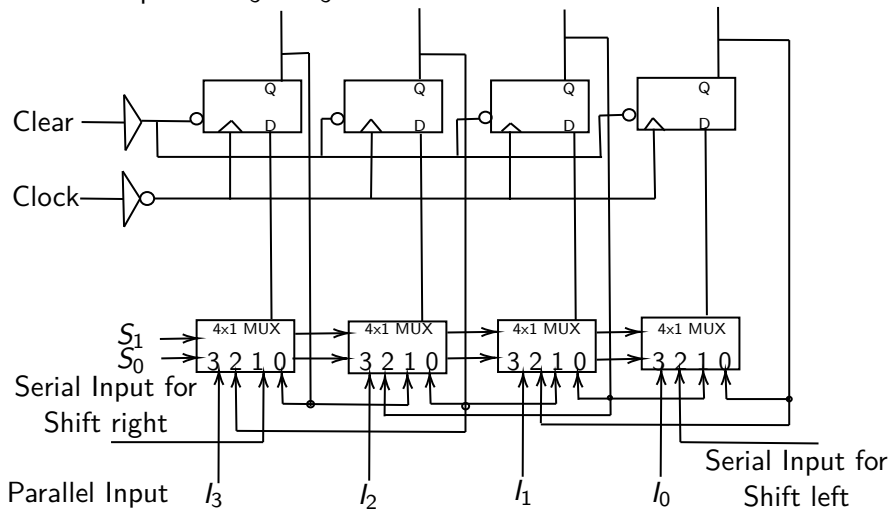Parallel Output $A_3 = A_3$ $A_2 = A_2$ $A_1 = A_1$ $A_0 = A_0$



Right Shift Universal Shift Register

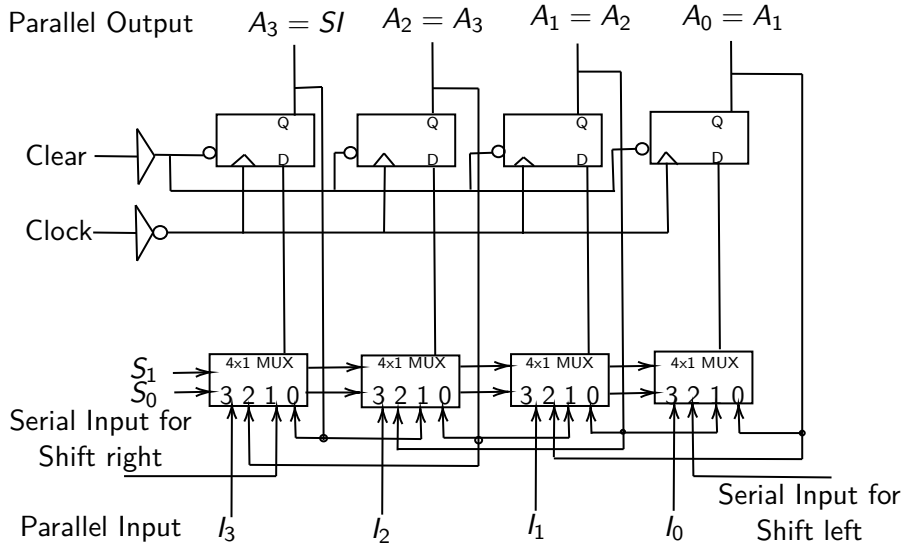
When $S_0 = 1$ and $S_1 = 0$, data will be shifted right.



Left Shift in Universal Shift Register


When $S_0 = 0$ and $S_1 = 1$, data will be shifted left.

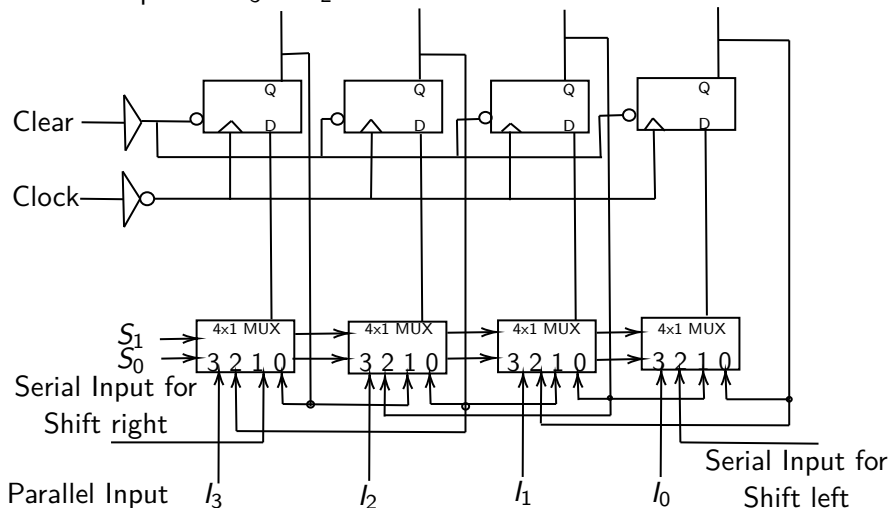Parallel Output $A_3 = A_2$ $A_2 = A_1$ $A_1 = A_0$ $A_0 = SI$



Parallel Load in Universal Shift Register

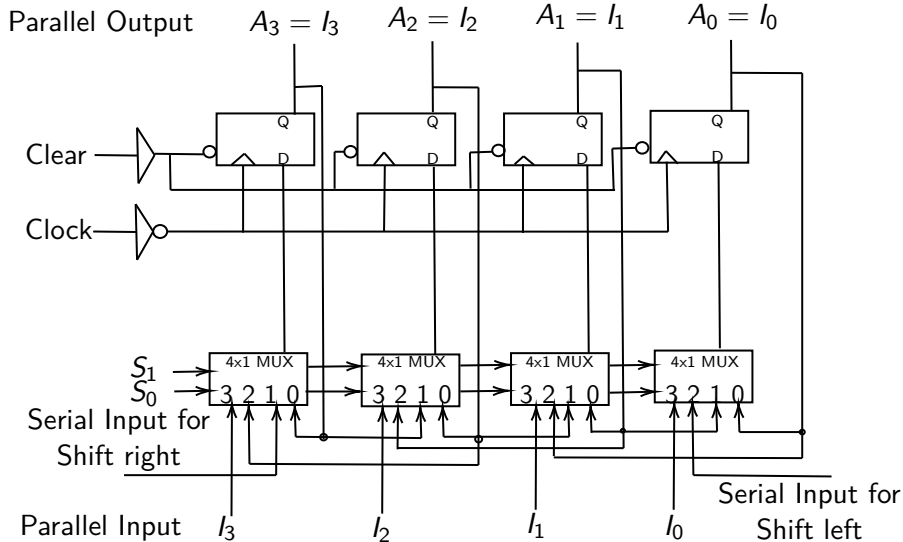When $S_0 = 1$ and $S_1 = 1$, data will be loaded from parallel input.



Purposes of Universal Shift Register

We can use **Universal Shift Register** in different purposes :

- Temporary data storage
- Data transfer
- Data manipulation
- As counters.

Uses of Universal Shift Register

In practical scenario , **Universal Shift Register** is used for

- Serial communication of micro controller unit
- Multiplying binary numbers
- Storing ALU's operands, intermediate results and final results

For performing **Universal Shift Register** operations,different ICs are used.

Example : IC 74194 (4 bit) and 74198 (8 bit)



Figure: IC 74194



Figure: IC 74198

Thank you!
Any Questions?